


Intro to ECSE Class 13:

1

Nodal Analysis Example Problems

I] Nodal Analysis with Current Sources

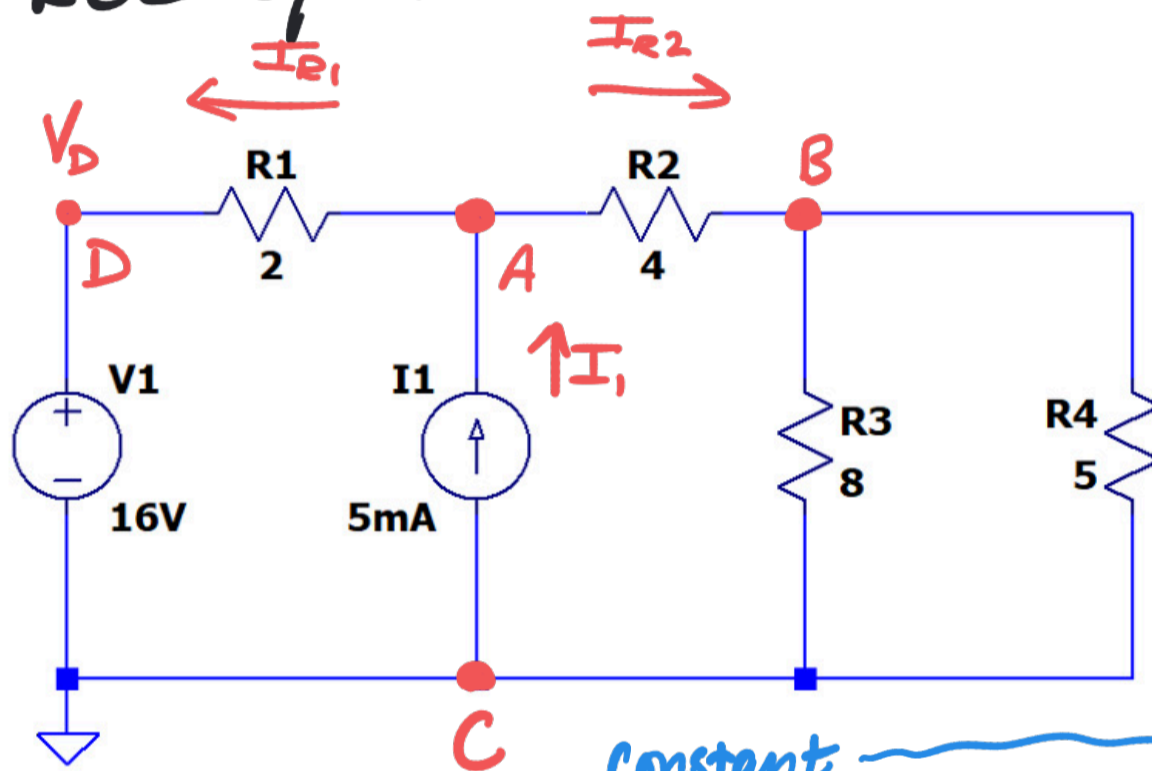- If we have a current source, it will appear as a constant current term in KCL equations



$$\text{KCL @ A: } \frac{V_A - V_D}{R_1} + \frac{V_A - V_B}{R_2} - I_1 = 0$$

in standard form:

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_A + \left(-\frac{1}{R_2}\right)V_B = I_1 + \frac{V_D}{R_1}$$


$$\left(\frac{1}{2\Omega} + \frac{1}{4\Omega}\right)V_A + \left(-\frac{1}{4\Omega}\right)V_B = 5 \times 10^{-3} \text{ A} + \frac{16\text{V}}{2\Omega}$$

II | Nodal Analysis with Multiple

2

Voltage Sources

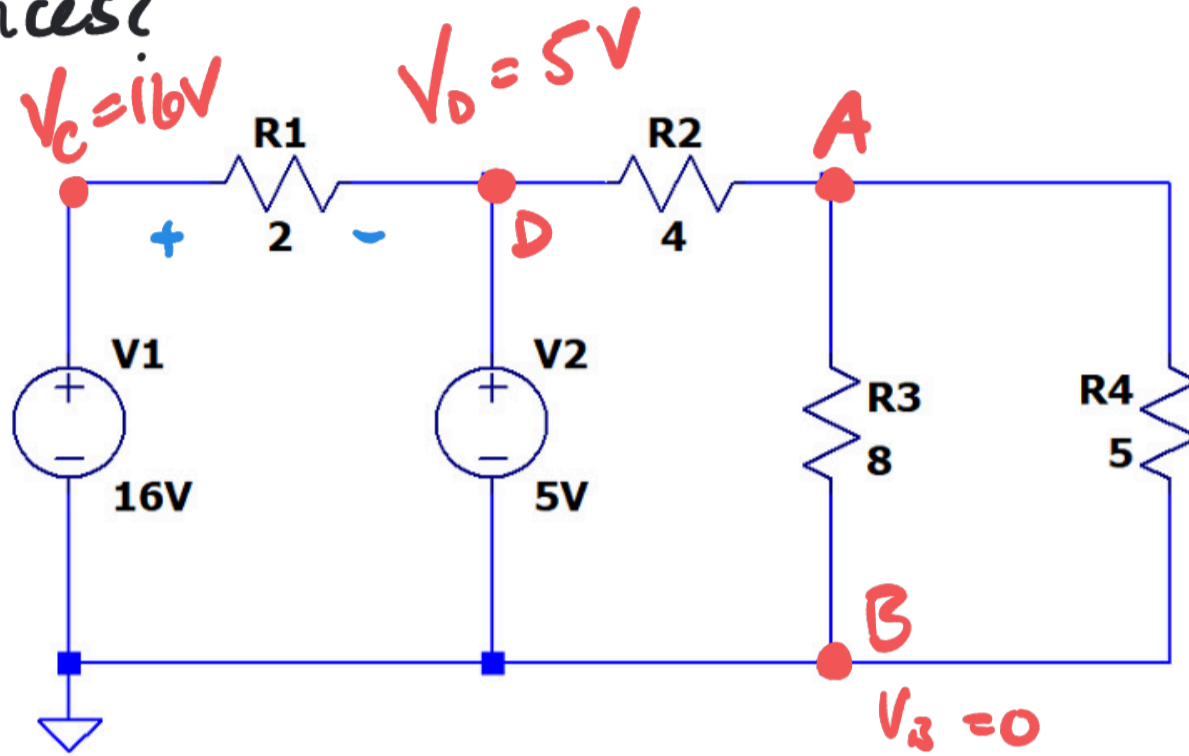- What happens if we have multiple voltage sources?




- # eqns = # nodes - # independent sources - 1

$$4 - 2 - 1 = 1 \text{ equation}$$

- effect: adding voltage sources to the circuit adds constraints to our system (we know the voltage at more nodes) and reduces the number of unknowns/equations

Example: What about this circuit?

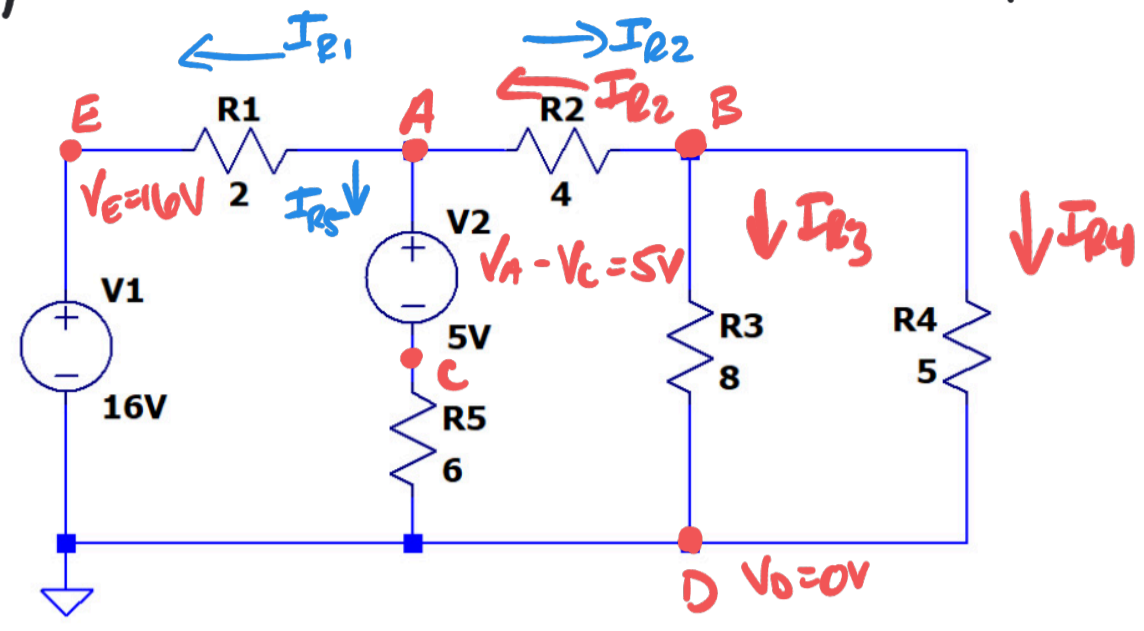

1. How many eqns? 5 total nodes - 2 voltage sources - 1 = 2 equations

Hint: How do we write I_{R5}? We know that the current flowing through the voltage source is the same as the current flowing through R₅ (they are in series)

equations: $V_A - V_C = 5V$ $V_D = 0$

① B: $\frac{V_B - V_A}{R_2} + \frac{V_B}{R_3} + \frac{V_B}{R_4} = 0$


A: $\frac{V_A - V_E}{R_1} + \frac{V_A - V_B}{R_2} + \frac{V_C}{R_5} = 0$

we know that $V_A - V_C = 5V \rightarrow V_C = V_A - 5V$

② $\frac{V_A - V_E}{R_1} + \frac{V_A - V_B}{R_2} + \frac{V_A - 5V}{R_5} = 0$

III | Dependent Sources

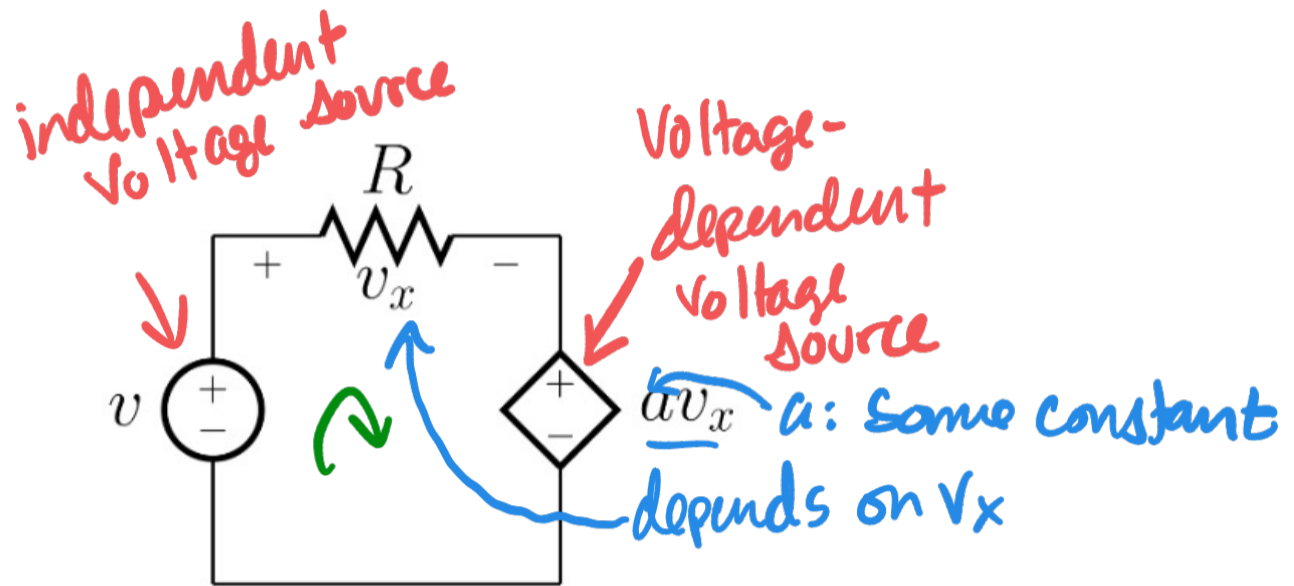- **Dependent Source:** has a value that's dependent on some other value in the circuit.



KVL: $-v + v_x + a v_x = 0$


- These aren't "real" sources like batteries - you can't buy one and put it in your circuit. They are used to create simple models of complicated circuits.

Types of dependent source


		Source Type	
		Voltage	Current
Depends on	Voltage	$V_s = a V_x$	$I_s = b V_x$
	Current	$V_s = c I_x$	$I_s = d I_x$

• Symbols

- dependent voltage source

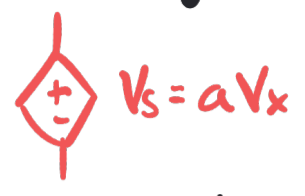


- dependent current source

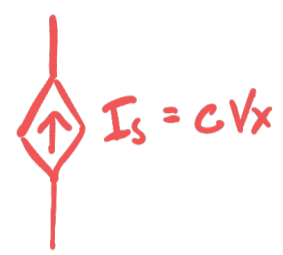

• Where do we use dependent sources?

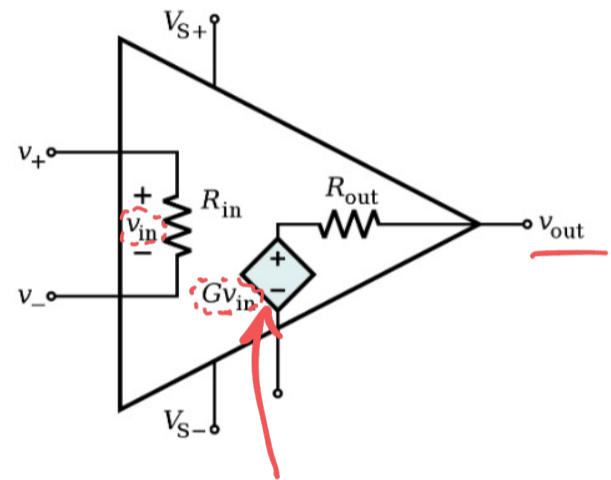
models of electronic devices or systems
operational amplifier model



- model says: v_{out} depends on a constant (G) times v_{in}


• Why model an op-amp like this?

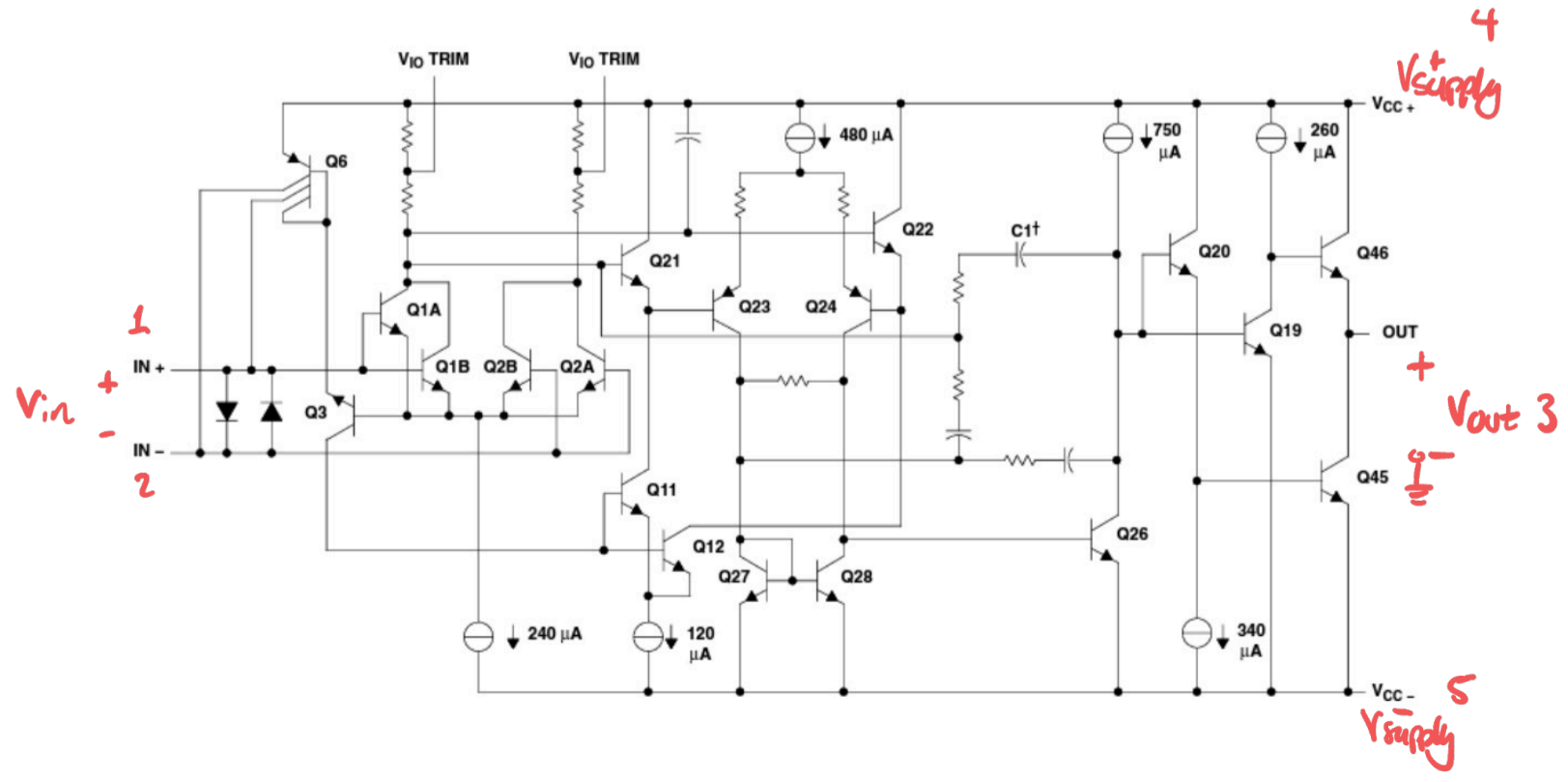- it describes the general behavior of an op-amp without having to analyze the whole circuit



IV | Extra Practice Problem

6

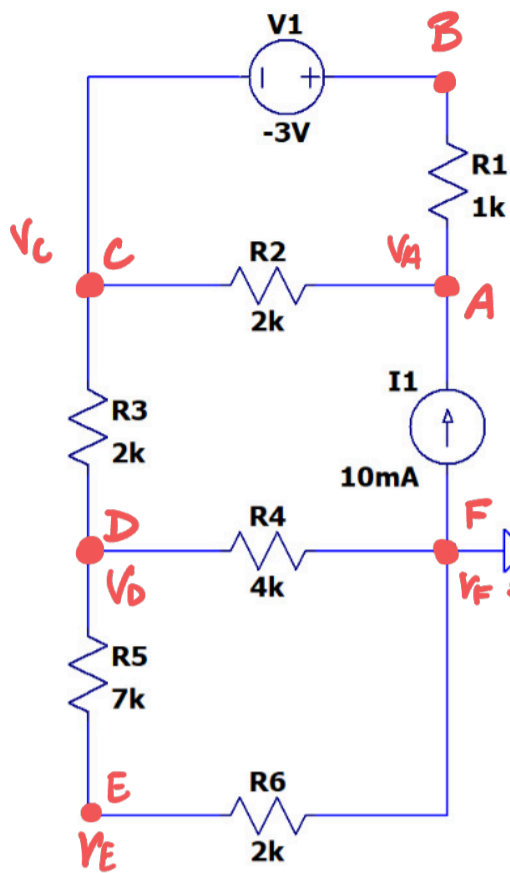

1) # nodes: 6

voltage sources: 1

unknowns: $6 - 1 - 1 = 4$

2) KCL equations + $V_B - V_C = -3V$

A: $\frac{V_A - V_B}{R_1} + \frac{V_A - V_C}{R_2} - I_1 = 0$

(1) $(\frac{1}{R_1} + \frac{1}{R_2})V_A + (-\frac{1}{R_1})V_B + (-\frac{1}{R_2})V_C = I_1$

C: $\frac{V_B - V_A}{R_1} + \frac{V_C - V_A}{R_2} + \frac{V_C - V_D}{R_3} = 0$

(2) $(-\frac{1}{R_1} - \frac{1}{R_2})V_A + (\frac{1}{R_1})V_B + (\frac{1}{R_2} + \frac{1}{R_3})V_C + (-\frac{1}{R_3})V_D = 0$

D: $\frac{V_D - V_C}{R_3} + \frac{V_D}{R_4} + \frac{V_D - V_E}{R_5} = 0$

(3) $(-\frac{1}{R_3})V_C + (\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5})V_D + (-\frac{1}{R_5})V_E = 0$

E: $\frac{V_E - V_D}{R_5} + \frac{V_E}{R_6} = 0$

(4) $(-\frac{1}{R_5})V_D + (\frac{1}{R_5} + \frac{1}{R_6})V_E = 0$

we can either substitute in $V_B = -3V + V_A$ everywhere and solve 4 equations OR keep our 4 equations as they are (in terms of V_A, V_B, V_C, V_D, V_E) and add a 5th equation: $V_B - V_C = -3V$ (5)

$$\begin{array}{l}
 1 \\
 2 \\
 3 \\
 4 \\
 5
 \end{array}
 \begin{bmatrix}
 (\frac{1}{1000} + \frac{1}{2000}) & (-\frac{1}{1000}) & (-\frac{1}{2000}) & 0 & 0 \\
 (-\frac{1}{1000} - \frac{1}{2000}) & (\frac{1}{1000}) & (\frac{1}{2000} + \frac{1}{2000}) & (-\frac{1}{2000}) & 0 \\
 0 & 0 & (-\frac{1}{2000}) & (\frac{1}{2000} + \frac{1}{4000} + \frac{1}{7000}) & (-\frac{1}{7000}) \\
 0 & 0 & 0 & (-\frac{1}{7000}) & (\frac{1}{7000} + \frac{1}{2000}) \\
 0 & 1 & -1 & 0 & 0
 \end{bmatrix}
 \begin{bmatrix}
 V_A \\
 V_B \\
 V_C \\
 V_D \\
 V_E
 \end{bmatrix}
 =
 \begin{bmatrix}
 10 \times 10^{-3} \\
 0 \\
 0 \\
 0 \\
 -3
 \end{bmatrix}
 \rightarrow
 \begin{cases}
 V_A = 52.36V \\
 V_B = 44.69V \\
 V_C = 47.69V \\
 V_D = 27.69V \\
 V_E = 6.15V
 \end{cases}$$

Upcoming Assignment Due Dates

7

1. Problem Set #5 Late Due Date: 10/16

2. Mid-Semester Survey Due Date: 10/16

3. Lab 02 Parts A & B Proof of Concepts
Due Date: 10/19

4. Problem Set #6

Due Date: 10/19