

# Exam 1 Crib Sheet

**Ohm's Law** – Linear relationship between voltage and current in a resistor

$$V = I R$$

V – Voltage, Volts [V]

I – Current, Amps [A]

R – Resistance, Ohms [ $\Omega$ ]


**Node** – a connection between two or more components

**Loop** – a closed path through which current can flow

**Power**

$$P = V I$$

P – Power, Watts [W]

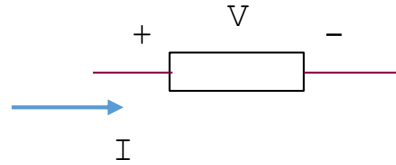

Using the above polarities (which may or be correct)


For  $P > 0$ , the component consumes power

For  $P < 0$ , the component produces power

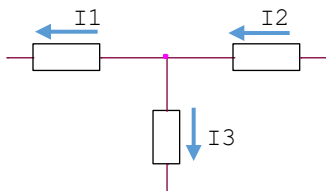**KCL – Kirchoff's Current Law**

$$\sum_{n=1}^N I_n = 0$$

The sum of the currents leaving a node is zero (signs determined by polarity).




$$I1 - I2 + I3 = 0$$

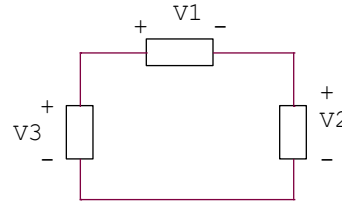**KVL – Kirchoff's Voltage Law**


$$\sum_{n=1}^N V_n = 0$$

The sum of the voltages around any closed loop is zero (signs determined by polarity).




$$V1 + V2 - V3 = 0$$

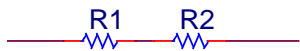**Resistors in series** –  $R_{EQ} = R1 + R2$



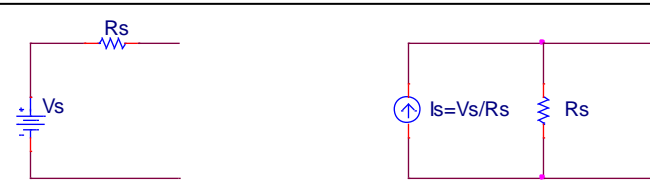**Resistors in parallel** -  $R_{EQ} = \left( \frac{1}{R1} + \frac{1}{R2} \right)^{-1}$



Source transformation

Voltage divider (two resistors in series)

$$V_{R1} = V_{source} \times \left[ \frac{R1}{R1 + R2} \right]$$

Current divider (two resistors in parallel)

$$I_{R1} = I_{source} \times \left[ \frac{R2}{R1 + R2} \right]$$

Superposition – For each **independent** source, turn off all other **independent** sources (**to turn off: Voltage source becomes a short circuit and Current source becomes an open circuit**) and find the contribution from that source. Sum the contribution from each source to get the parameter of interest.

# Exam 1 Crib Sheet

**Node Analysis**

# of KCL Equations = Total # of nodes – voltage sources -1

**Mesh Analysis**

# of KVL Equations = Total # mesh loops – current sources

$$\frac{V_A}{R1} + \frac{V_A - V_B}{R3} = 0$$

$$\frac{V_B}{R2} + \frac{V_B - V_A}{R3} - I_1 + \frac{V_C}{R4} = 0$$

$$V_C - V_B = 2000I_x$$

$$\frac{V_B}{R2} = I_x$$

$$(i_1)R1 + (i_1)R3 + (i_1 - i_2)R2 = 0$$

$$-2000I_x + (i_3)R4 + (i_2 - i_1)R2 = 0$$

$$i_3 - i_2 = I_1$$

$$i_1 - i_2 = I_x$$

Example includes a Current Controlled Voltage Source (CCVS) as a dependent source and I1 as an independent source.

Thevenin voltage ( $V_{TH}$ ) – **Open** circuit the load, find the voltage across the load nodes  
 Norton current ( $I_N$ )– **Short** circuit the load, find the current through that short circuit  
 Thevenin resistance ( $R_{TH}$ ) – Turn off all **independent** sources, replace the load with a test voltage ( $V_{test}$ ), find the current ( $I_{test}$ ) through the test voltage,  $R_{TH} = V_{test}/I_{test}$ .

$V_{TH} = I_N R_{TH}$  (Ohm's Law relationship)

**Comparator**

If  $V1 < V2$ ,  $V_{out} = V^+_{saturation}$   
 If  $V1 > V2$ ,  $V_{out} = V^-_{saturation}$

**Inverting amplifier circuit**

$V_{out} = -\frac{R2}{R1} V_{in}$

Ideal op amp equations  
 $I_N = I_p = 0$  no current draw  $R_{in} = \infty$   
 $V_p = V_n$  ( $A \rightarrow \infty$ )  
 $R_{out} = 0$

**Non-inverting amplifier circuit**

$V_{out} = \left(1 + \frac{R2}{R1}\right) V_{in}$

**Summing amplifier circuit**


$V_{out} = -\frac{Rf}{R1} V1 - \frac{Rf}{R2} V2$

## Exam 2 Crib Sheet

### IV Characteristics – Time domain


**Resistors –**

$$V(t) = I(t)R$$

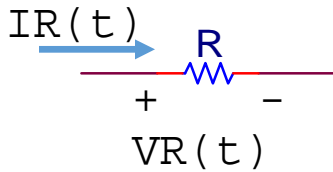


**Inductors –**

$$V_L(t) = L \frac{dI_L}{dt}$$

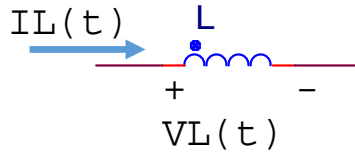

**Capacitors –**

$$I_C(t) = C \frac{dV_C}{dt}$$

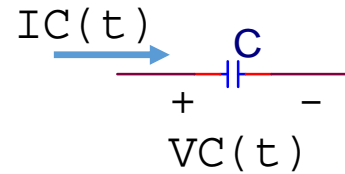

### Continuity conditions

$$I_L(t_o^-) = I_L(t_o^+)$$

$$V_C(t_o^-) = V_C(t_o^+)$$

### IV Characteristics – Laplace domain


$$Z_R = R$$

$$Z_L = sL$$

$$Z_C = \frac{1}{sC}$$



**Resistors –**

$$V(s) = Z_R I(s)$$

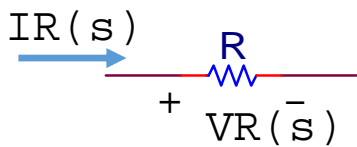



**Inductors –**

$$V_L(s) = Z_L I_L(s) - LI(0^+)$$

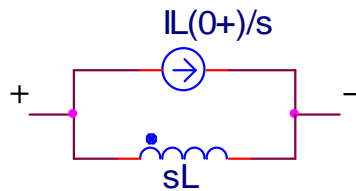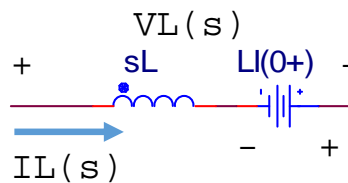

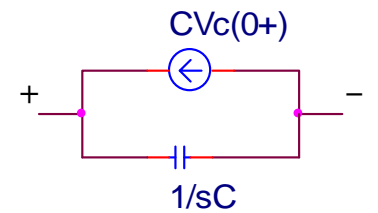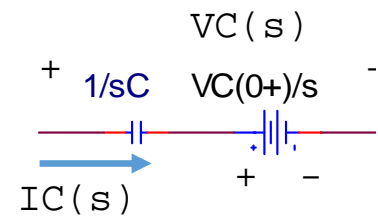**Capacitors –**

$$V_C(s) = Z_C I_C(s) + \frac{V_C(0^+)}{s}$$



**Impedance,  $Z [\Omega]$ , properties have the same characteristics as resistance**

**Impedances in series add,  $Z_{EQ} = Z_1 + Z_2$**

**Impedances in parallel have an inverse relationship,  $Z_{EQ} = \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right)^{-1} = \frac{Z_1 Z_2}{Z_1 + Z_2}$**

Initial Value Theorem  $\lim_{s \rightarrow \infty} \{sF(s)\} = f(t=0^+)$

Final Value Theorem  $\lim_{s \rightarrow 0} \{sF(s)\} = f(t \rightarrow \infty)$

## Exam 2 Crib Sheet

### First order circuits

Differential equation:  $\tau \frac{dy}{dt} + y = f(t)$ , with solution  $y(t) = y_h(t) + y_p(t)$

$f(t)$  represents a source function or  $n^{\text{th}}$  derivative of the source function, with appropriate coefficients

$y_h(t)$  represents the homogeneous/transient part of the solution

For first order circuits, the homogeneous solution always takes the form  $y_h(t) = Ae^{-\frac{t}{\tau}}$

$y_p(t)$  represents the particular/forced part of the solution.

The particular solution is always the same type of function as the source.

$\tau$  is the time constant

For RC circuits,  $\tau = RC$

For RL circuits,  $\tau = L/R$

### Second order circuits

Differential equation:  $\frac{d^2y}{dt^2} + 2\alpha \frac{dy}{dt} + \omega_o^2 y = f(t)$ , with solution  $y(t) = y_h(t) + y_p(t)$

s-domain  $s^2Y(s) + 2\alpha sY(s) + \omega_o^2 Y(s) = F(s)$

$y_h(t)$  represents the homogeneous/transient part of the solution

The form of the homogeneous solution depends on the damping

$y_p(t)$  represents the particular/forced part of the solution.

The particular solution is always the same type of function as the source.

$f(t)$  represents a source function or  $n^{\text{th}}$  derivative of the source function

$F(s)$  represents the Laplace transform of the function  $f(t)$

<b>Overdamped</b> ( $\alpha > \omega_o$ )	$y_h(t) = A_1 e^{-\alpha_1 t} + A_2 e^{-\alpha_2 t}$	$-\alpha_1, -\alpha_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2}$
	$y(0^+) = A_1 + A_2 + y_p(0^+)$	$\frac{dy(0^+)}{dt} = -\alpha_1 A_1 - \alpha_2 A_2 + \frac{dy_p(0^+)}{dt}$
<b>Critically Damped</b> ( $\alpha = \omega_o$ )	$y_h(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$	$\alpha$ from the differential equation
	$y(0^+) = A_1 + y_p(0^+)$	$\frac{dy(0^+)}{dt} = -\alpha A_1 + A_2 + \frac{dy_p(0^+)}{dt}$
<b>Underdamped</b> ( $\alpha < \omega_o$ )	$y_h(t) = e^{-\alpha t} [A_1 \cos(\beta t) + A_2 \sin(\beta t)]$	$\alpha$ from the differential equation $\beta = \sqrt{\omega_o^2 - \alpha^2}$
	$y(0^+) = A_1 + y_p(0^+)$	$\frac{dy(0^+)}{dt} = -\alpha A_1 + \beta A_2 + \frac{dy_p(0^+)}{dt}$
RLC series circuit	$\alpha = \frac{1}{2} \frac{R}{L} \quad \omega_o = \frac{1}{\sqrt{LC}}$	RLC parallel circuit $\alpha = \frac{1}{2} \frac{1}{RC} \quad \omega_o = \frac{1}{\sqrt{LC}}$

# Exam 2 Crib Sheet

## Partial Fraction Expansion

### Simple Real Poles:

In General:

$$\text{Expand: } F(s) = \frac{A_1}{s-p_1} + \frac{A_2}{s-p_2} + \frac{A_3}{s-p_3} + \dots$$

$$A_n = [(s-p_n)F(s)]|_{s=p_n}; \quad \text{Cover-Up Rule}$$

$$\Rightarrow f(t) = (A_1 e^{p_1 t} + A_2 e^{p_2 t} + A_3 e^{p_3 t} + \dots) \quad t \geq 0$$

### Real, Equal Poles – Double Pole:

- Real, Equal Poles – Double Pole:

$$\text{Expand } F(s) = \frac{A_1}{s-p_1} + \dots + \left[ \frac{A_{n1}}{s-p_n} + \frac{A_{n2}}{(s-p_n)^2} \right]$$

$$A_{n2} = \left[ (s-p_n)^2 F(s) \right] |_{s=p_n}; \quad \text{Cover-Up Rule}$$

Usually Find  $A_{n1}$  from evaluating  $F(0)$  or  $F(1)$

$$\Rightarrow f(t) = (A_1 e^{p_1 t} + \dots + A_{n1} e^{p_n t} + A_{n2} t e^{p_n t}) \quad t \geq 0$$

Simple Poles      Repeated Poles

### Complex Conjugate Poles

In General:

$$\text{Expand } F(s) = \frac{A_1}{s-p_1} + \dots + \frac{A}{s+\alpha-j\beta} + \frac{A^*}{s+\alpha+j\beta}$$

Find  $A_1$  and  $A = |A|/\phi$  from Cover-Up Rule

$$\Rightarrow f(t) = A_1 e^{p_1 t} + \dots + 2|A| e^{-\alpha t} \cos(\beta t + \phi) \quad t \geq 0$$

Simple Poles      Complex Poles

## LAPLACE TRANSFORMS

Signal	$f(t)$	$F(s)$
Impulse	$\delta(t)$	1
Step	$u(t)$	$\frac{1}{s}$
Constant	$Au(t)$	$\frac{A}{s}$
Ramp	$tu(t)$	$\frac{1}{s^2}$

seeyes@rpi.edu

www.rpi.edu/seeyes



## LAPLACE TRANSFORMS

Signal	$f(t)$	$F(s)$
Exponential	$e^{-\alpha t}u(t)$	$\frac{1}{s+\alpha}$
Damped Ramp	$[te^{-\alpha t}]u(t)$	$\frac{1}{(s+\alpha)^2}$
Cosine Wave	$[\cos\beta t]u(t)$	$\frac{s}{s^2+\beta^2}$
Damped Cosine	$[e^{-\alpha t}\cos\beta t]u(t)$	$\frac{s+\alpha}{(s+\alpha)^2+\beta^2}$

seeyes@rpi.edu

www.rpi.edu/seeyes



## LAPLACE TRANSFORMS

Time Domain	s-Domain
$Af_1(t) + Bf_2(t)$	$AF_1(s) + BF_2(s)$
$\int_0^t f(\tau) d\tau$	$\frac{F(s)}{s}$
$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
$e^{-\alpha t}f(t)$	$F(s+\alpha)$
$t f(t)$	$-dF(s)/ds$
$f(t-a)u(t-a)$	$e^{-as}F(s)$

seeyes@rpi.edu

www.rpi.edu/seeyes




# LAPLACE TRANSFORMS

<u>Signal</u>	<u>Time Domain</u>	<u>S Domain</u>
Impulse	$\delta(t)$	1
Step	$u(t)$	$s^{-1}$
Constant	$Au(t)$	$As^{-1}$
Ramp	$tu(t)$	$s^{-2}$
Exponential	$e^{-\alpha t}u(t)$	$(s + \alpha)^{-1}$
Damped ramp	$te^{-\alpha t}u(t)$	$(s + \alpha)^{-2}$
Cosine	$\cos(\beta t)u(t)$	$\frac{s}{s^2 + \beta^2}$
Damped cosine	$e^{-\alpha t}\cos(\beta t)u(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \beta^2}$
Sum	$Af_1(t) + Bf_2(t)$	$Af_1(s) + Bf_2(s)$
Integral	$\int_0^t f(\tau)d\tau$	$s^{-1}f(s)$
Derivative	$\frac{df(t)}{dt}$	$sf(s) - f(0^-)$
Exponential $\times$ function	$e^{-\alpha t}f(t)$	$f(s + \alpha)$
$t \times$ function	$tf(t)$	$-\frac{df(s)}{ds}$
Shifted function	$f(t - a)u(t - a)$	$e^{-as}f(s)$

**NOTATION:**  $\mathcal{L}\{f(t)\}(s) = f(s)$  and  $\mathcal{L}^{-1}\{f(s)\}(t) = f(t)$

# Exam 3 Crib Sheet

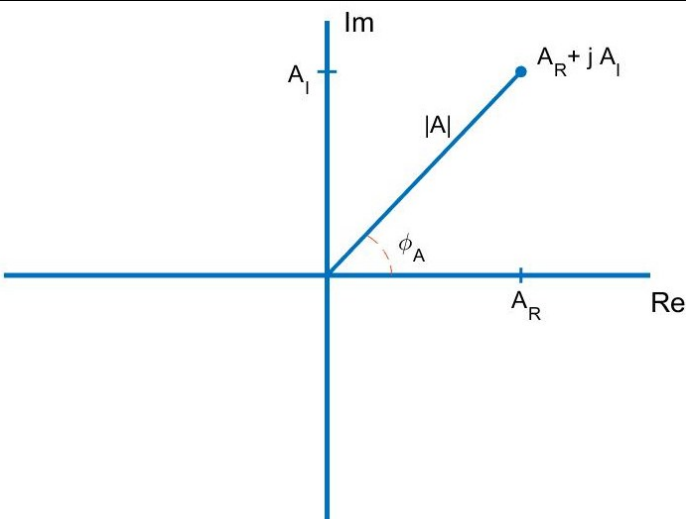
Complex Numbers		
	<p>Rectangular form:  <math>A = A_R + jA_I</math></p> <p>Polar form:  <math> A  \angle \varphi_A</math></p> <p>Rectangular to polar  <math> A  = \sqrt{(A_R)^2 + (A_I)^2}</math>  <math>\varphi_A = \tan^{-1} \left( \frac{A_I}{A_R} \right)</math></p> <p>Polar to rectangular  <math>A_R =  A  \cos(\varphi_A)</math>  <math>A_I =  A  \sin(\varphi_A)</math></p>	
Euler's Law: $e^{j\theta} = \cos(\theta) + j \sin(\theta)$		
Mathematics with complex number		
<p><b>Addition/Subtraction – Rectangular form</b></p> $A + B = (A_R + B_R) + j(A_I + B_I)$ $A - B = (A_R - B_R) + j(A_I - B_I)$ <p>Complex conjugate  <math>A = A_R + jA_I \quad A^* = A_R - jA_I</math></p>	<p><b>Multiplication/Division – Rectangular form</b></p> $AB =  A  B  \angle (\varphi_A + \varphi_B)$ $\frac{A}{B} = \frac{ A }{ B } \angle (\varphi_A - \varphi_B)$ <p>Complex conjugate  <math>A =  A  \angle \varphi_A \quad A^* =  A  \angle -\varphi_A</math></p>	
AC Steady State signals		
<p><b>Time domain signals</b></p> $F(t) = A_o \cos(\omega t + \theta)$ <p><math>A_o</math> – amplitude  <math>\omega</math> – radial frequency, <math>2\pi f</math>  <math>\Theta</math> – phase</p>	<p><b>Phasor signals</b></p> $\tilde{F} = A_o \angle \theta$ <p><math>A_o</math> – amplitude  <math>\Theta</math> – phase</p>	
(Rectangular form) $F(t) = A_o \cos(\omega t + \theta) \leftrightarrow A_o \Re\{e^{j(\omega t + \theta)}\} \leftrightarrow A_o e^{j\theta} \leftrightarrow A_o \angle \theta$ (Phasor form)		
Impedances – Laplace domain (zero initial conditions)		
$Z_R = R$	$Z_L = sL$	$Z_C = \frac{1}{sC}$
Impedances – AC steady state		
$Z_R = R$ $Z_R = R \angle 0^\circ$	$Z_L = j\omega L$ $Z_L = \omega L \angle 90^\circ$	$Z_C = \frac{1}{j\omega C}$ $Z_C = \frac{1}{\omega C} \angle -90^\circ$
Impedance, $Z [\Omega]$ , properties have the same characteristics as resistance		
<i>In series</i> add, $Z_{EQ} = Z_1 + Z_2$		<i>In parallel</i> , inverse relationship, $Z_{EQ} = \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right)^{-1} = \frac{Z_1 Z_2}{Z_1 + Z_2}$
Admittance, $Y [mho]$ , properties have characteristics that are the 'inverse' of impedance		
<i>In parallel</i> , add, $Y_{EQ} = Y_1 + Y_2$		<i>In series</i> , inverse relationship, $Y_{EQ} = \left( \frac{1}{Y_1} + \frac{1}{Y_2} \right)^{-1} = \frac{Y_1 Y_2}{Y_1 + Y_2}$
AC Steady State Power		
$S = P + jQ$ S – Complex power	Using Ohm's Law relationships for impedances (Z)	

## Exam 3 Crib Sheet


<p>P – Real power, [W] Q – Reactive power, [VAR]   S  – Apparent Power, [VA]</p>	$P = I_{RMS}^2  Z  \cos \theta$ $= I_{RMS}^2 R(\omega)$ $= V_{RMS} I_{RMS} \cos \theta$ <p style="text-align: right;">{ Equivalent ways of expressing Real Power [Watts]</p> $Q = I_{RMS}^2  Z  \sin \theta$ $= I_{RMS}^2 X(\omega)$ $= V_{RMS} I_{RMS} \sin \theta$ <p style="text-align: right;">{ Equivalent ways of expressing Reactive Power [VAR's]</p> <p>If using <math>V_{RMS}^2</math> version of equations also divide by <math> Z </math> (phasor form) *cos or sin <math>\theta</math> OR must use complex conjugate of Z (rectangular form)</p>
<p>Capacitive reactance is negative (<math>Q &lt; 0</math>)</p> <p>Inductive reactance is positive (<math>Q &gt; 0</math>)</p> <p>Power produced by the source(s) is equal to the sum of the power produced/stored for each impedance in the circuit</p>	<p>Power factor – a metric over how efficient power consumption/production appears to be</p> <p style="text-align: center;"><math>0 &lt; \text{power factor} &lt; 1</math></p> <p style="text-align: center;">Power factor = <math>\frac{P}{ S } = \cos(\phi_S)</math></p>

### Power Triangle

## POWER TRIANGLE

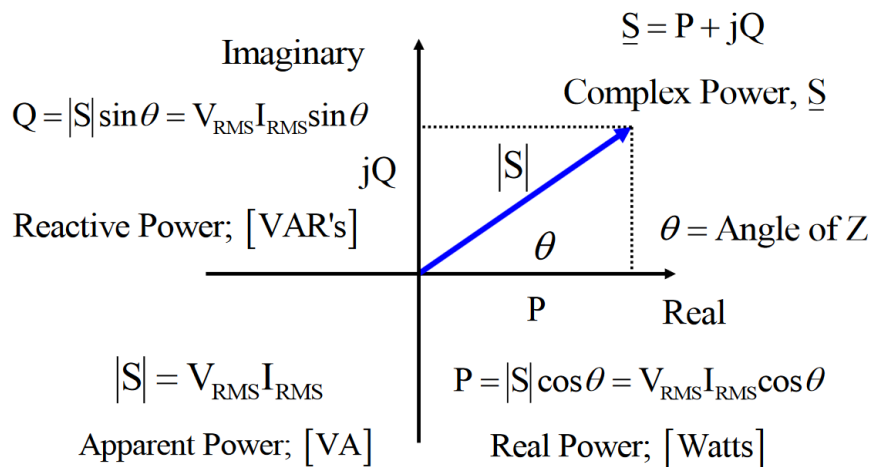


### Ideal Transformers

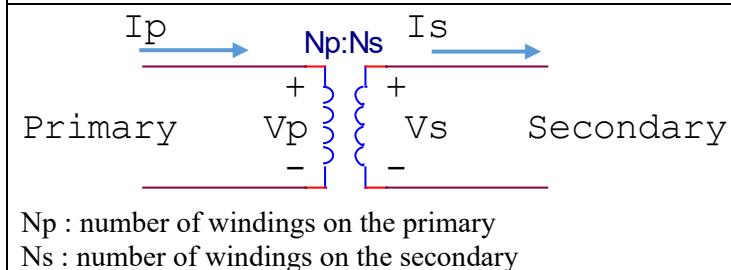


Primary: source side of the transformer  
Secondary: load side of the transformer  
The winding ratio,  $N = \frac{N_s}{N_p}$   
Voltage relationship,  $V_s = N V_p$   
Current relationship,  $I_s = \frac{I_p}{N}$



## Exam 3 Crib Sheet

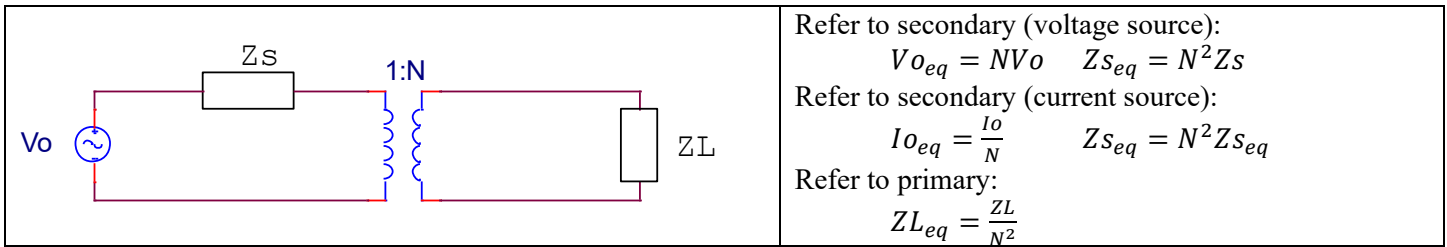


### Mutual Inductance

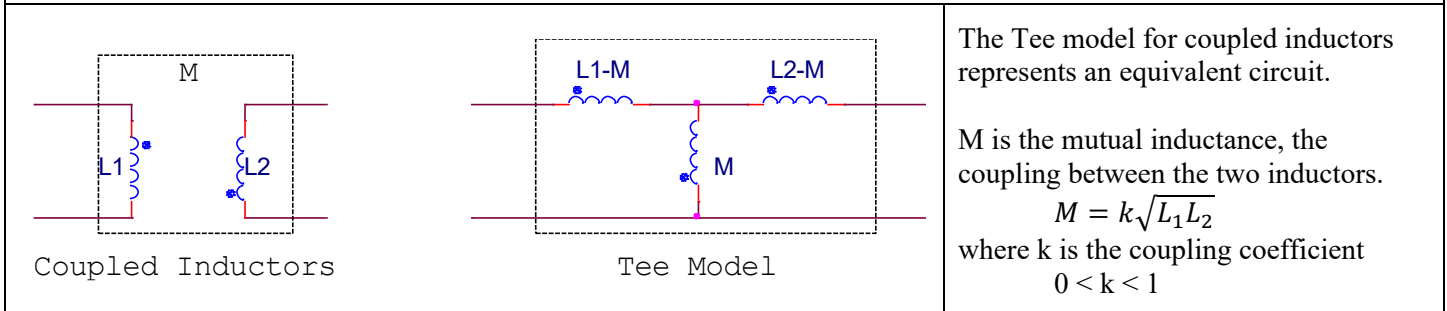


### Student Requested Add-ons

### REFERRAL TO PRIMARY

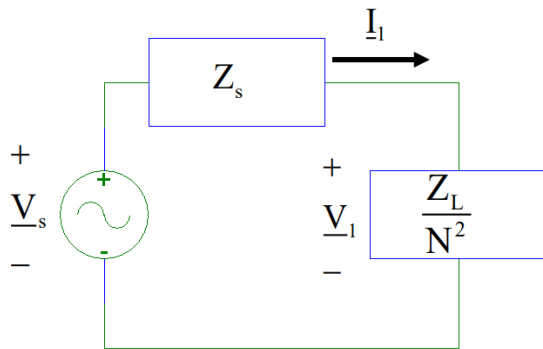


### REFERRAL TO SECONDARY

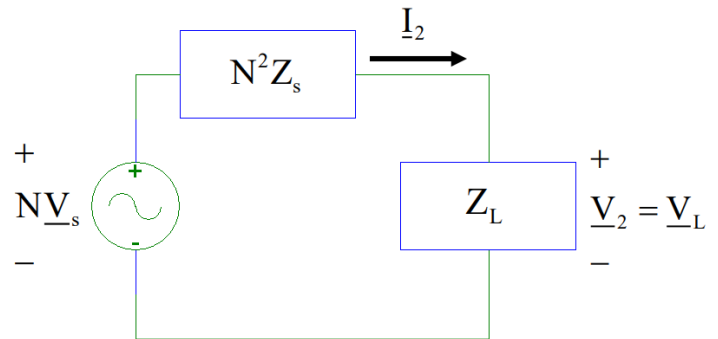

<i>Complex Power</i>	
$P = I_{RMS}^2  Z  \cos\theta$	$Q = I_{RMS}^2  Z  \sin\theta$
$P = I_{RMS}^2 R(\omega)$	$Q = I_{RMS}^2 X(\omega)$
$P = V_{RMS} I_{RMS} \cos\theta$	$Q = V_{RMS} I_{RMS} \sin\theta$
<i>Notes</i>	
$R(\omega) = Z_{REAL}$	$X(\omega) = Z_{IMG}$
$\theta = \text{Angle of Impedance}$	$\theta = \tan^{-1}\left(\frac{Z_{IMG}}{Z_{REAL}}\right)$
$\theta > 0 \Rightarrow I \text{ lags } V \text{ (Ind.)}$	$\theta < 0 \Rightarrow I \text{ leads } V \text{ (Cap.)}$

# Bode Plots Crib Sheet

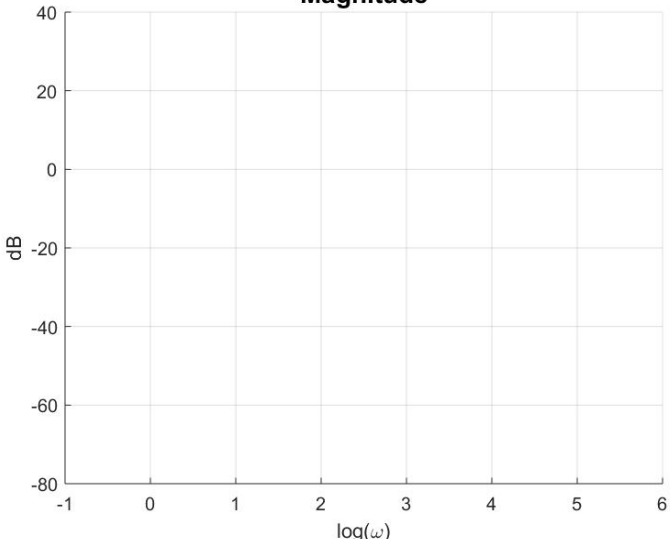Bode Plots	
<div style="text-align: center; font-weight: bold; margin-bottom: 10px;">Magnitude</div> 	<p>Decade – a change in frequency by one order of magnitude, for example            100 rad/s → 1000 rad/s            10<sup>4</sup> Hz → 10<sup>5</sup> Hz</p> <p>dB – decibel  <math>dB = 20 \log  F(j\omega) </math>            Note the argument of the logarithm is a magnitude expression</p> <p>A change of 20dB corresponds to a of <math> F(j\omega) </math> by one order of magnitude</p>
Bode plot magnitude approximations	
$H(s) \propto s^n$	Slope +20dB/decade
$H(s) \propto \frac{1}{s^n}$	Slope -20dB/decade
$H(s) \propto K$	‘Flat’, dB = 20log K
Sketching Bode plot magnitudes (real poles and zeros)	
Crossing an n-pole: Slope <b>changes</b> by -20*n dB/decade  Crossing an n-zero: Slope <b>changes</b> by +20*n dB/decade	‘n’ indicates the number of poles or zeros  ‘Crossing’ rules apply when going from a lower frequency to a higher frequency
Sketching Bode plot phases (real poles and zeros)	
Crossing an n-pole: Phase <b>changes</b> by $-n * \frac{\pi}{2}$  Crossing an n-zero: Phase <b>changes</b> by $+n * \frac{\pi}{2}$	Phase changes are ‘spread out’ over two decades, one decade on either side of the pole or zero
Corrections for Bode plot magnitudes (real poles and zeros)	
At an n-pole: The ‘real’ dB valule is -3n dB ‘below’ the asymtote  At an n-zero: The ‘real’ dB valule is +3n dB ‘above’ the asymtote	The asymptote is the straight line approximation of the Bode plots  ‘Far away’ from poles and zeros, the asymptotes are an accurate representation of the Bode plot

## Bode Plots Crib Sheet

Second Order Circuits	
Damping ratio, $\delta = \frac{\alpha}{\omega_o}$ , a metric of the damping $\alpha$ is the attenuation constant $\omega_o$ is the resonant frequency	$\delta > 1$ , overdamped  $\delta = 1$ , critically damped  $\delta < 1$ , underdamped
<p>Lowpass/Highpass filters</p> <p style="margin-left: 20px;">Overdamped and critically damped cases, the Bode plots follow the procedure on the previous page</p> <p style="margin-left: 20px;">Underdamped cases, use the critically damped approximation, add a ‘correction’ of <math>20 \log \left  \frac{1}{2\delta} \right </math> at the resonant frequency, <math>\omega_o</math></p> <p>Bandpass filters</p> <p style="margin-left: 20px;">Overdamped, the Bode plots follow the procedure on the previous page</p> <p style="margin-left: 20px;">Critically damped and underdamped cases</p> <p style="margin-left: 40px;">At the resonant frequency, the magnitude Bode plot is 0dB</p> <p style="margin-left: 40px;">The vertex where the stopbands meet is <math>20 \log  2\delta </math></p> <p><i>Note: The above discussion is for second order circuits only. If there is a gain stage, the Bode plot moves ‘up’ or ‘down’ and the dB value of the gain determines the reference for adding corrections/stopband vertices</i></p>	
Cascaded Filters – Magnitude Bode Plots	
$H(s) = H_1(s)H_2(s)H_3(s)$ (three stages) $\rightarrow$ $\text{dB} = 20\log H_1(j\omega)H_2(j\omega)H_3(j\omega)  = 20\log H_1(j\omega)  + 20\log H_2(j\omega)  + 20\log H_3(j\omega) $ $\text{angle} = \angle [H_1(j\omega)H_2(j\omega)H_3(j\omega)] = \angle H_1(j\omega) + \angle H_2(j\omega) + \angle H_3(j\omega)$	

# Bode Plots Crib Sheet

First order filters

$$\omega_c = \frac{1}{RC} \qquad \omega_c = \frac{R}{L}$$


Filter name

Schematic(s)

H(s)


pole/zero ID

Low pass filter

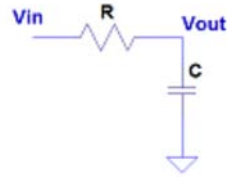


$$\frac{\omega_c}{s + \omega_c}$$

1 pole

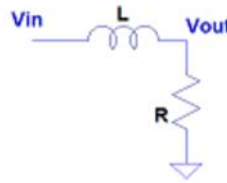

High pass filter

$$\omega_c = \frac{1}{RC}$$

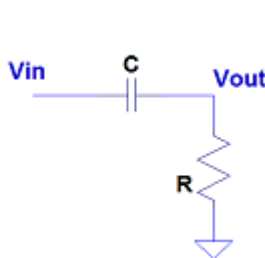


$$\frac{s}{s + \omega_c}$$

1 zero at zero

1 pole

$$\omega_c = \frac{R}{L}$$

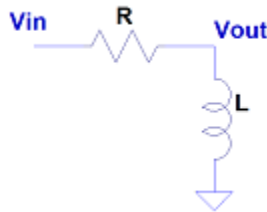

# Bode Plots Crib Sheet

## Second order filters

Filter name	Schematic(s)	H(s)	pole/zero ID
Low pass filter		$\frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2}$	2 poles
High pass filter		$\frac{s^2}{s^2 + 2\alpha s + \omega_0^2}$	2 zeros at zero 2 poles
Bandpass filter		$\frac{2\alpha s}{s^2 + 2\alpha s + \omega_0^2}$	1 zero at zero 2 poles
Bandstop filter		$\frac{s^2 + \omega_0^2}{s^2 + 2\alpha s + \omega_0^2}$	