

# ELECTRIC CIRCUITS ECSE-2010

Lecture 23: Review



## LECTURE 18.1 REVIEW

- Transfer Functions
- Phasors
- Phasor Math



## TRANSFER FUNCTIONS

H(s) = One of the most important things we can find for a circuit

H(s) depends only the circuit

H(s) does **NOT** depend on the Input


Find H(s) by ASSUMING there is no Initial Stored Energy

and then finding the Ratio of  $\frac{\text{Output}(s)}{\text{Input}(s)}$

Will use H(s) to find the Frequency Response of a Circuit



## PHASORS

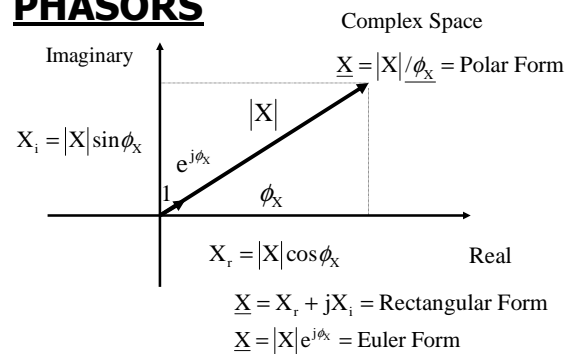

## PHASORS

- **Phasors are Complex Numbers:**
  - Need to Use Complex Math
  - Will Use Complex Math Instead of Solving Differential Equations or Using Laplace Transforms to Find Amplitude and Phase Changes between AC Input and AC Steady State Output



## PHASORS

- **Phasors are Complex Numbers:**
  - Will Find that Equations Relating Current Phasors,  $\underline{I}$ , and Voltage Phasors,  $\underline{V}$  for R, L and C will be Linear and Algebraic
  - Can Use All Techniques from Unit I to Solve Circuits in the AC Steady State



## PHASORS

- 3 Ways to Express Phasors

Rectangular Form;  $\underline{X} = X_r + jX_i$

Polar Form;  $\underline{X} = |X| / \phi_x$

Euler Form;  $\underline{X} = |X| e^{j\phi_x}$

- Will Need to Be Able to Easily Convert Between the 3 Different Forms



## COMPLEX MATH

- **Addition:**

$$\begin{aligned} \cdot \underline{A} + \underline{B} &= (a_r + j a_i) + (b_r + j b_i) \\ &= (a_r + b_r) + j (a_i + b_i) \end{aligned}$$

- **Subtraction:**

$$\begin{aligned} \cdot \underline{A} - \underline{B} &= (a_r + j a_i) - (b_r + j b_i) \\ &= (a_r - b_r) + j (a_i - b_i) \end{aligned}$$

- => **Do Addition/Subtraction in Rectangular Form**



## COMPLEX MATH

- **Multiplication:**

- **Difficult to do in Rectangular Form**

- **Use Euler or Polar Form**

$$\begin{aligned} \underline{A} \times \underline{B} &= A e^{j\phi_1} \times B e^{j\phi_2} = AB e^{j(\phi_1 + \phi_2)} \\ &= A / \phi_1 \times B / \phi_2 = AB / (\phi_1 + \phi_2) \end{aligned}$$



## COMPLEX MATH

- **Division:**

$$\begin{aligned} \underline{A} \div \underline{B} &= A e^{j\phi_1} / B e^{j\phi_2} = \frac{A}{B} e^{j(\phi_1 - \phi_2)} \\ &= A / \phi_1 / B / \phi_2 = \frac{A}{B} / (\phi_1 - \phi_2) \end{aligned}$$

- **Do Multiplication/Division in Polar Form or Euler Form**



## RATIONALIZATION

- **Division in Rectangular Form:**

$$\underline{C} = \underline{A} \div \underline{B} = \frac{a_r + ja_i}{b_r + jb_i}$$

Want to express as  $\underline{C} = C_r + jC_i$

Multiply  $\frac{a_r + ja_i}{b_r + jb_i}$  by  $\frac{b_r - jb_i}{b_r - jb_i}$

$$\begin{aligned} \Rightarrow \underline{C} &= \frac{a_r b_r + a_i b_i}{b_r^2 + b_i^2} + j \frac{a_i b_r - a_r b_i}{b_r^2 + b_i^2} \\ &= C_r + j C_i \end{aligned}$$



## LECTURE 19.1 AGENDA

- Kirckoff's laws for phasors
- AC steady state impedance



### K'S LAWS FOR PHASORS

- **Circuit in AC steady state:**

$$\text{Input} = x(t) = |X| \cos(\omega t + \phi_x)$$

Express  $x(t)$  as a Phasor  $\underline{X} = |X| / \phi_x$

- **Can express all v's and i's in circuit as phasors:**

$$v_1(t) \rightarrow \underline{V}_1; v_2(t) \rightarrow \underline{V}_2$$

$$i_1(t) \rightarrow \underline{I}_1; i_2(t) \rightarrow \underline{I}_2$$



### K'S LAWS FOR PHASORS

- **KCL:**

- If  $i_1 + i_2 = i; \Rightarrow \underline{I}_1 + \underline{I}_2 = \underline{I}$

- **KVL:**

- If  $v_1 + v_2 = v; \Rightarrow \underline{V}_1 + \underline{V}_2 = \underline{V}$

- **K's Laws Work for Phasors!**

- **Complex Addition, not Simple Addition**



### AC STEADY STATE IMPEDANCE


- **Capacitor:**

$$i_c = C \frac{dv_c}{dt}$$

$$v_c(t) = V \cos(\omega t + \phi)$$

$$= \text{Real} [V e^{j(\omega t + \phi)}]$$
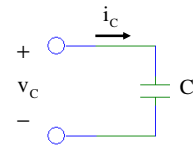
$$= \text{Real} [V e^{j\phi} e^{j\omega t}] = \text{Real} [\underline{V}_c e^{j\omega t}]$$



### AC STEADY STATE IMPEDANCE


- **Capacitor:**

$$i_c = C \frac{dv_c}{dt}$$

$$v_c(t) = V \cos(\omega t + \phi)$$

$$= \text{Real} [V e^{j(\omega t + \phi)}]$$
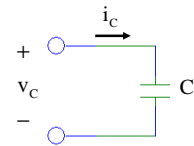
$$= \text{Real} [V e^{j\phi} e^{j\omega t}] = \text{Real} [\underline{V}_c e^{j\omega t}]$$



### AC STEADY STATE IMPEDANCE


- **Inductor:**

$$v_L = L \frac{di_L}{dt}$$

$$i_L(t) = I \cos(\omega t + \phi)$$

$$= \text{Real} [I e^{j(\omega t + \phi)}]$$
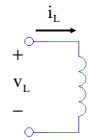
$$= \text{Real} [I e^{j\phi} e^{j\omega t}] = \text{Real} [\underline{I}_L e^{j\omega t}]$$



### AC STEADY STATE IMPEDANCE

$$Z_R = R \Omega$$

$$Z_L = j\omega L \Omega$$

$$Z_C = -\frac{j}{\omega C} = \frac{1}{j\omega C} \Omega$$



## AC STEADY STATE IMPEDANCE

Note:

As  $\omega \rightarrow 0$ ;  $Z_L = j\omega L \rightarrow 0$

Inductor is a Short Circuit for DC

As  $\omega \rightarrow \infty$ ;  $Z_L = j\omega L \rightarrow \infty$

Inductor is an Open Circuit for

Very High Frequencies



## AC STEADY STATE IMPEDANCE

Note:

As  $\omega \rightarrow 0$ ;  $Z_C = -\frac{j}{\omega C} \rightarrow \infty$

Capacitor is an Open Circuit for DC

As  $\omega \rightarrow \infty$ ;  $Z_C = -\frac{j}{\omega C} \rightarrow 0$

Capacitor is a Short Circuit for

Very High Frequencies



## AC STEADY STATE IMPEDANCE

■ In General,  $\underline{V} = \underline{Z} \underline{I}$  in AC Steady State:

•  $\underline{Z}$  = AC SS Impedance

• Units of Ohms

• Ohm's Law for AC Steady State

■  $\underline{Y}$  = AC Steady State Admittance

=  $1/\underline{Z}$  (Units of mhos)



## AC STEADY STATE IMPEDANCE

$\underline{V} = \underline{Z} \underline{I}$ ; Ohm's Law for AC Steady State

$\underline{Z} = R(\omega) + jX(\omega)$  = AC Steady State Impedance

$R(\omega)$  = AC Steady State Resistance

$X(\omega)$  = AC Steady State Reactance

$\underline{Y} = G(\omega) + jB(\omega)$  = AC Steady State Admittance

$G(\omega)$  = AC Steady State Conductance

$B(\omega)$  = AC Steady State Susceptance




## LECTURE 20.1 AGENDA

- AC Thevenin/Norton circuits
- AC node equations
- AC mesh equations
- AC bridge circuits




## EQUIVALENT IMPEDANCE

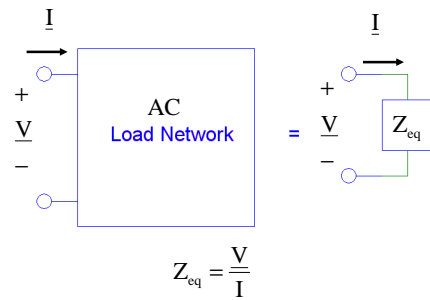

$$Z_{eq} = \frac{V}{I}$$



## AC THEVENIN/NORTON

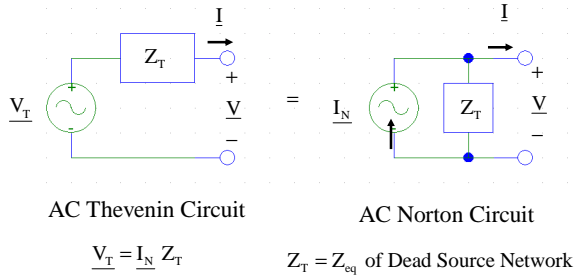


sawyes@rpi.edu

www.rpi.edu/~sawyes



## AC SOURCE CONVERSIONS

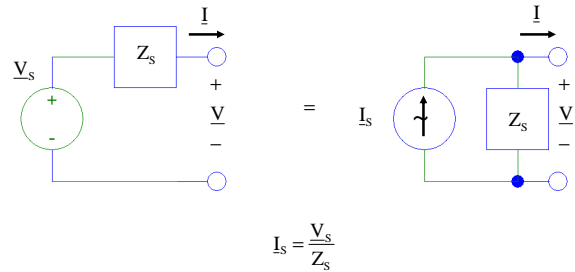

sawyes@rpi.edu

www.rpi.edu/~sawyes



## AC NODE EQUATIONS

Technique to Solve Any AC Steady State Circuit

1. Label Unknown Phasor Node Voltages,  $\underline{V}_1, \underline{V}_2$ , etc.
2. # Unknown Nodes = # Nodes - # Voltage Sources - 1 (Reference)
3. Write a KCL at Each Unknown Node
4. Sum of Phasor Currents OUT of Node = 0
5. Relate Phasor Currents to Phasor Node Voltages using Ohm's Law for AC Steady State
6. Will Always Get the Same Number of Equations as Unknowns
7. Solve Complex Linear Equations for  $\underline{V}_1, \underline{V}_2$ , etc.

sawyes@rpi.edu

www.rpi.edu/~sawyes



## AC MESH EQUATIONS

Technique to Solve Any AC Steady State Circuit


1. Define All Phasor Mesh Currents
  1. Unknown Mesh Currents ( $\underline{I}_1, \underline{I}_2, \underline{I}_3$ , etc.) and Current Sources (Independent and Controlled)
2. Write KVL around Each Unknown Mesh
3. Sum of Phasor Voltages around Mesh = 0
4. Relate Phasor Voltages to Phasor Mesh Currents using Ohm's Law for AC Steady State
5. Will Always get Same Number of Equations as Unknowns
6. Solve Complex Linear Equations for  $\underline{I}_1, \underline{I}_2, \underline{I}_3$ , etc.

sawyes@rpi.edu

www.rpi.edu/~sawyes



## IMPEDANCE BRIDGES

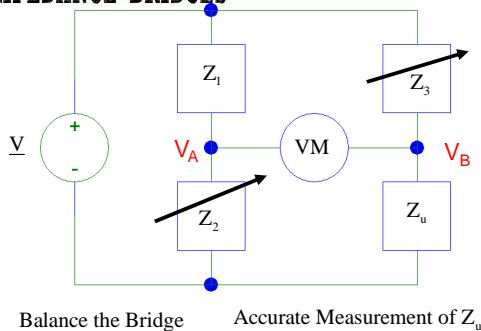

sawyes@rpi.edu

www.rpi.edu/~sawyes



## IMPEDANCE BRIDGES

Parallel voltage dividers

$$\underline{V}_M = \underline{V}_A - \underline{V}_B = \left( \frac{Z_2}{Z_1 + Z_2} \right) \cdot \underline{V}_S - \left( \frac{Z_u}{Z_3 + Z_u} \right) \cdot \underline{V}_S$$

$$\underline{V}_M = \left[ \frac{Z_2 \cdot Z_3 - Z_1 \cdot Z_u}{(Z_1 + Z_2) \cdot (Z_3 + Z_u)} \right] \cdot \underline{V}_S$$


VM is zero when  $Z_2 Z_3 = Z_1 Z_u$

$$Z_{u} = \frac{Z_2 \cdot Z_3}{Z_1} = R_X + jX_X$$

sawyes@rpi.edu

www.rpi.edu/~sawyes



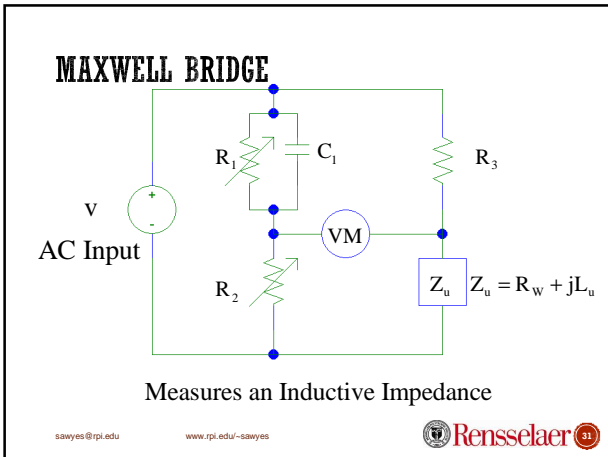

### IMPEDANCE BRIDGES

- Why 2 Variable Impedances?:
  - Must balance Resistance and Reactance of the Circuit
  - Amplitude and Phase of  $\underline{I}_m, \underline{V}_m$
  - Real and Imaginary Parts of  $\underline{I}_m, \underline{V}_m$

sawyes@rpi.edu    www.rpi.edu/~sawyes    Rensselaer 32

### LECTURE 21.1

- Review AC Power
  - Complex Power
  - Real Power
  - Reactive Power
  - Apparent Power
- Power Factor

sawyes@rpi.edu    www.rpi.edu/~sawyes    Rensselaer 33

### REACTIVE POWER

Define  $P = \text{"Real Power"} = V_{\text{RMS}} I_{\text{RMS}} \cos \theta$   
 $P$  is Measured in Watts

Define  $Q = \text{"Reactive Power"} = V_{\text{RMS}} I_{\text{RMS}} \sin \theta$   
 $Q$  is Measured in VAR's  
 (Volt-Amperes-Reactive)

sawyes@rpi.edu    www.rpi.edu/~sawyes    Rensselaer 34

### REACTIVE POWER

- $Q$  is a Measure of the Rate of Change of Energy Stored in the Reactive Elements (L, C):
  - Power companies must worry about  $Q$  since they supplied this energy
  - Supplied  $Q$  over their Lines => Real Cost
  - Power companies want customers to have Low  $Q$

sawyes@rpi.edu    www.rpi.edu/~sawyes    Rensselaer 35

### REACTIVE POWER

$$P = I_{\text{RMS}}^2 |Z| \cos \theta$$

$$= I_{\text{RMS}}^2 R(\omega)$$

$$= V_{\text{RMS}} I_{\text{RMS}} \cos \theta$$

{ Equivalent ways of expressing Real Power  
[Watts]

$$Q = I_{\text{RMS}}^2 |Z| \sin \theta$$

$$= I_{\text{RMS}}^2 X(\omega)$$

$$= V_{\text{RMS}} I_{\text{RMS}} \sin \theta$$

{ Equivalent ways of expressing Reactive Power  
[VAR's]

sawyes@rpi.edu    www.rpi.edu/~sawyes    Rensselaer 36

## REACTIVE POWER

### ■ Notes on Reactive Power:

- Real Power = P is always  $\geq 0$
- Reactive Power = Q can be  $\geq 0$  or  $\leq 0$
- For Inductive Load,  $X > 0 \Rightarrow Q > 0$
- For Capacitive Load,  $X < 0 \Rightarrow Q < 0$



## COMPLEX POWER

Define "Complex Power" =  $\underline{S} = P + jQ$

$\underline{S}$  is a Complex Number, but not a Phasor

$\underline{S}$  is a Convenient Way to Keep Track of P and Q

Real $\{\underline{S}\} = P = V_{\text{RMS}} I_{\text{RMS}} \cos \theta \Rightarrow$  Watts

Imag $\{\underline{S}\} = Q = V_{\text{RMS}} I_{\text{RMS}} \sin \theta \Rightarrow$  VAR's



## APPARENT POWER


Magnitude of  $\underline{S} = |\underline{S}| = \sqrt{P^2 + Q^2} = V_{\text{RMS}} I_{\text{RMS}}$

$|\underline{S}| =$  "Apparent Power"  $\Rightarrow$  [Volt-Amperes]


$|\underline{S}| =$  Product of  $V_{\text{RMS}}$  x  $I_{\text{RMS}}$  at Terminals



## POWER TRIANGLE

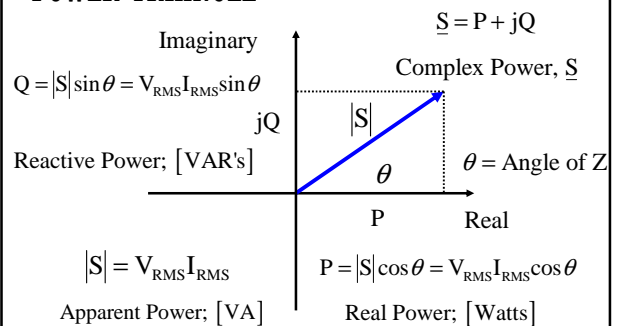

## POWER FACTOR

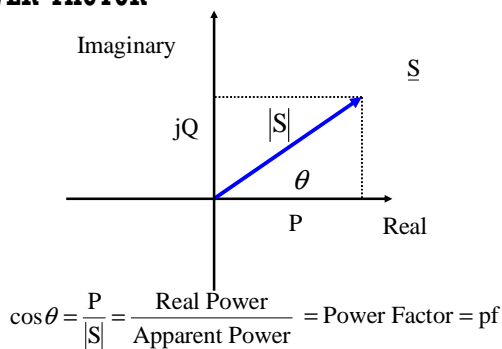

## POWER FACTOR

For Inductive Loads,  $\theta > 0$ ;  $\cos \theta > 0$

For Capacitive Loads,  $\theta < 0$ ;  $\cos \theta > 0$

Need a Way to Distinguish

$$\underline{I} = \frac{\underline{V}}{\underline{Z}} = \frac{|\underline{V}| \angle \phi}{|\underline{Z}| \angle \theta} = \frac{|\underline{V}|}{|\underline{Z}|} \angle \phi - \theta$$

If  $\theta > 0$ ;  $\Rightarrow$  Lagging Power Factor ( $\underline{I}$  lags  $\underline{V}$ )

If  $\theta < 0$ ;  $\Rightarrow$  Leading Power Factor ( $\underline{I}$  leads  $\underline{V}$ )



## POWER FACTOR

Power Factor:

Define  $\text{pf} = \cos \theta$ ;  $0 \leq \text{pf} \leq 1$


Must distinguish between  $\theta \geq 0$ ,  $\theta \leq 0$ :

$\theta \geq 0$ ;  $X \geq 0$ ;  $Q \geq 0$ ;  $\underline{I}$  lags  $\underline{V}$ ; lagging pf

$\theta \leq 0$ ;  $X \leq 0$ ;  $Q \leq 0$ ;  $\underline{I}$  leads  $\underline{V}$ ; leading pf

e.g: pf = .8 lagging  $\Rightarrow$  Inductive Load

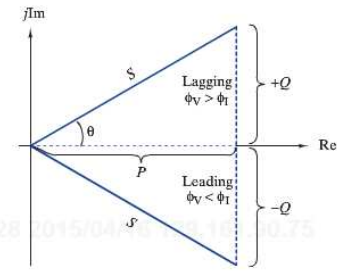pf = .8 leading  $\Rightarrow$  Capacitive Load



$P > 0$ , net energy is transferred from source to load ( $P < 0$ ?)  
Lagging (inductive) 1<sup>st</sup> quadrant  
Leading (capacitive) 4<sup>th</sup> quadrant

sawyes@rpi.edu

www.rpi.edu/~sawyes



## LECTURE 22.1


- Coupled Inductors
- Ideal Transformer
- Transformer Circuit
- Power Transfer
- Impedance Matching
- Mutual Inductance (Tee Model)

sawyes@rpi.edu

www.rpi.edu/~sawyes



## TRANSFORMER CIRCUIT

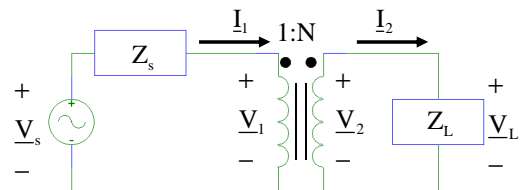

2 Choices for the Equivalent Circuit

Refer Secondary Circuit to the Primary

OR


Refer Primary Circuit to the Secondary

sawyes@rpi.edu

www.rpi.edu/~sawyes



## REFERRAL TO PRIMARY

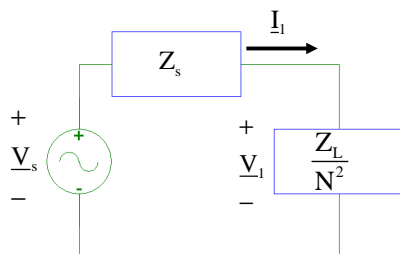

Equivalent to Basic Transformer Circuit


Can Now Do AC Steady State Circuit Analysis

sawyes@rpi.edu

www.rpi.edu/~sawyes



## REFERRAL TO SECONDARY

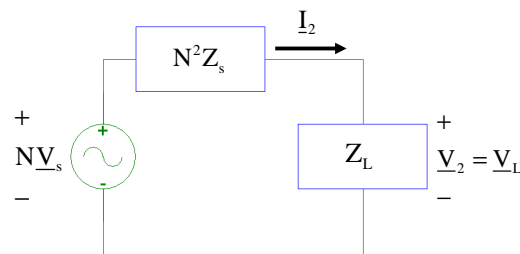

Equivalent to Basic Transformer Circuit


Can Now Do AC Steady State Circuit Analysis

sawyes@rpi.edu

www.rpi.edu/~sawyes



## POWER TRANSFER

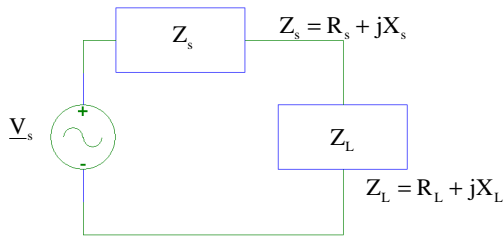


For Maximum Power to  $Z_L$ , Choose  $Z_L = Z_s^*$   
 $\Rightarrow R_L = R_s$  and  $X_L = -X_s$

sawyes@rpi.edu

www.rpi.edu/~sawyes



## MUTUAL INDUCTANCE

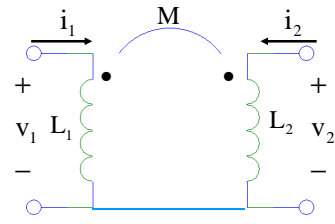


$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



## MUTUAL INDUCTANCE

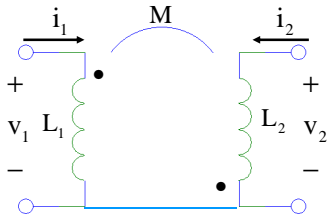


$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



## MUTUAL INDUCTANCE

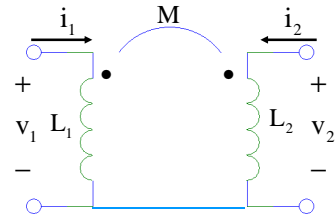

Would Like to Replace with  
 an Equivalent Circuit that does  
 NOT have any Mutual Inductance




## TEE MODEL

■ Consider a Circuit That Looks Like a "Tee":

- 3 Ideal Inductors
- No Mutual Inductance




## TEE MODEL

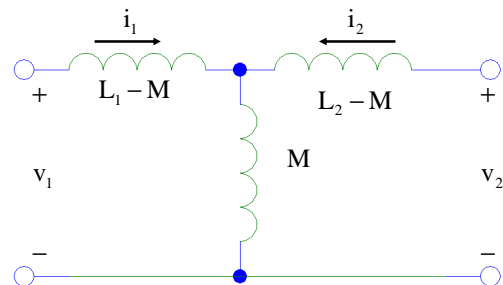

No Coupling Between Inductors



### TEE MODEL

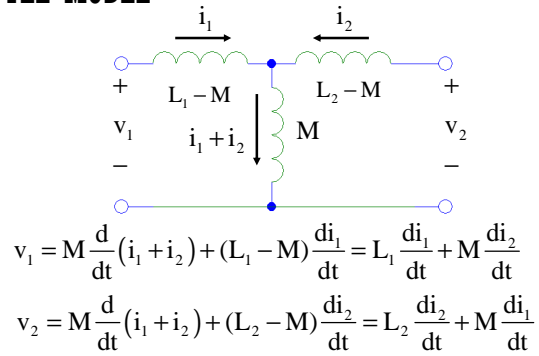


### TEE MODEL

- For a "Tee" Circuit:
  - 3 Ideal Inductors, No Mutual Inductance
  - Same Equations as Before
- => Can Replace Inductors exhibiting Mutual Inductance with "Tee Model" and then do AC Steady State Circuit Analysis :



### TEE MODEL

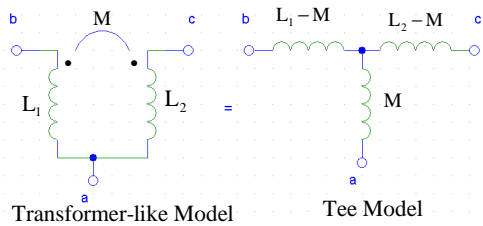

If Dots on Opposite Sides =>  $M \rightarrow -M$

Some Inductors in Tee Model May Be Negative!

